

"familiarize with three state buffer registers connected to the bus".

Objectives:

- i) To know about three state buffer register
- ii) To know about registers connected to bus.
- iii) To implement 4-bit RTL
- iv) To perform different types of operation.

Introduction In digital electronics three state, tri state, logic allows an output or input to assume a high impedance state, effectively removing the output from the circuit, in addition to the 0 and 1 logic levels, this allows multiple circuits to share the same output line or lines.

Table 1:

1 Truth table normally open.

| ENABLE | Din | Pout |
|--------|-----|------|
| 0 | X | Open |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

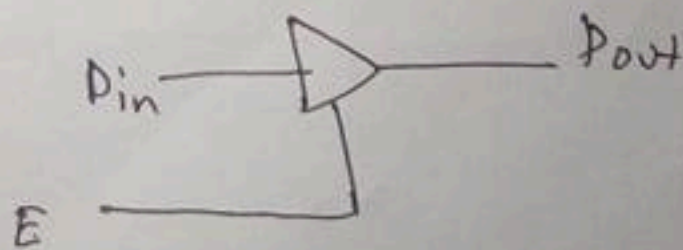


Fig 1: Normally open.

Table 2: Normally closed

| DISABLE | Din | Pout |
|---------|-----|------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | X | Open |

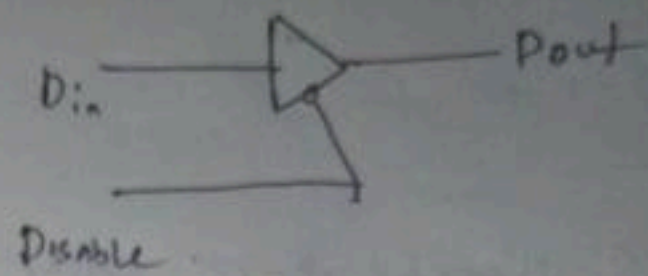


fig 2: normally closed switch.

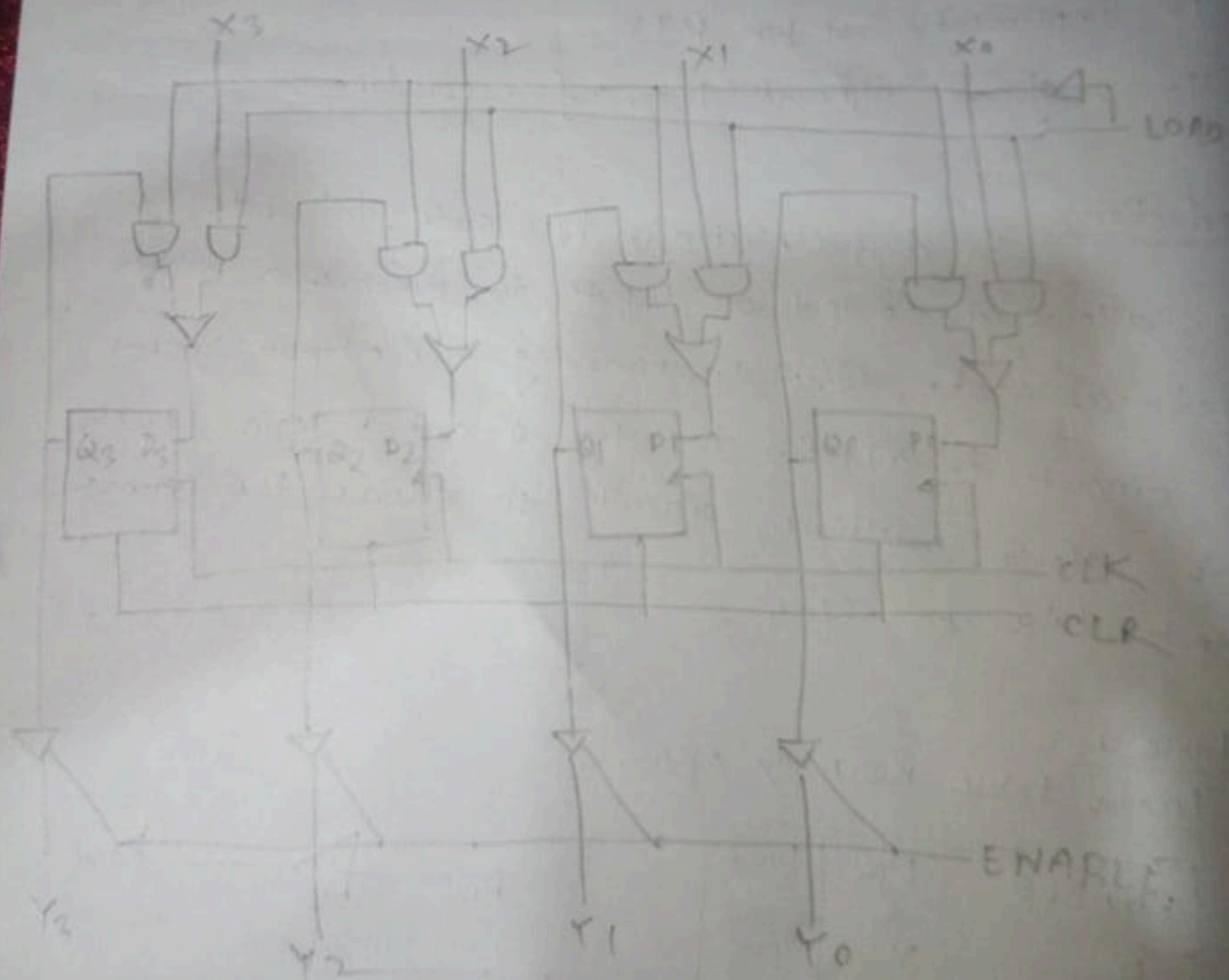


figure 3: three state buffer register

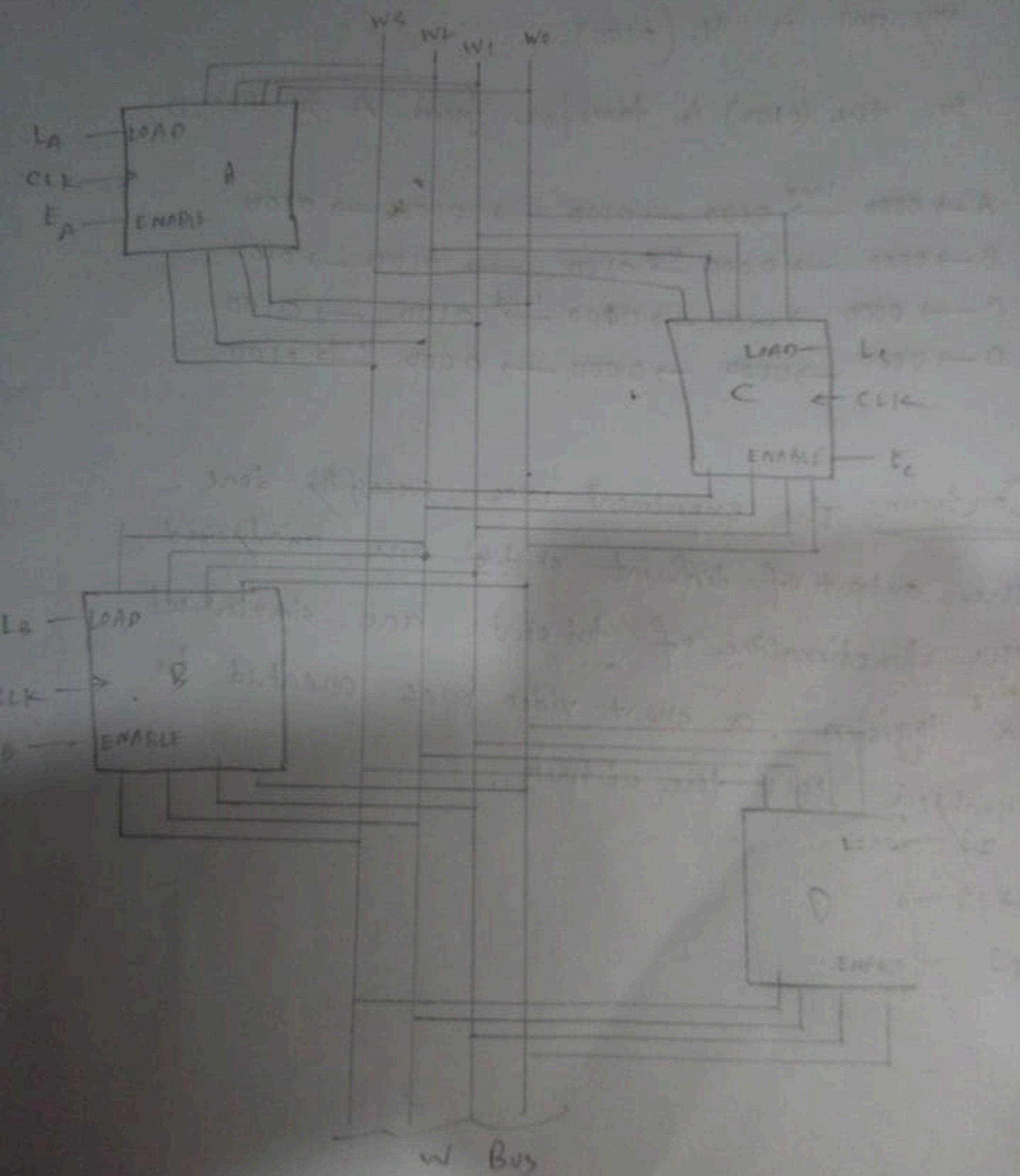


Fig 4: Register connected to Bus.

Discussion my roll is 1607048. a digit of
my roll is 4. (0100).

So, the (0100) is transfer from A to B, C, D.

A \rightarrow 0000 $\xrightarrow{\text{load}}$ 0100 \rightarrow 0100 \rightarrow 0100 \rightarrow 0100
 B \rightarrow 0000 \rightarrow 0000 $\xrightarrow{\text{load}}$ 0100 \rightarrow 0100 \rightarrow 0100
 C \rightarrow 0000 \rightarrow 0000 \rightarrow 0000 $\xrightarrow{\text{load}}$ 0100 \rightarrow 0100
 D \rightarrow 0000 \rightarrow 0000 \rightarrow 0000 \rightarrow 0000 $\xrightarrow{\text{load}}$ 0100

Conclusion: The experiment was successfully done.
 The output of different status are analysed.
 The functionalities of tri state are simulated
 in logisim. a short video was created to
 visualize all the outputs.